

Lab 3: Finite State Machine: Vending Machine

Ethan Ngo

TA: Ananya Ravikumar (Section 3)

May 23, 2021

Contents

1	Introduction	3
2	Module Description	4
3	Test-bench Simulation	8
4	Reports	12
4.1	ISE Design Overview Summary Report	12
4.2	Map Report	12
5	Conclusion	16

1 Introduction

The focus of this lab is to learn about finite state machines and directly implementing these ideas and behaviors through the design of a vending machine. Finite State Machines (FSMs) are very useful in a wide variety of real world systems. An FSM has some finite number of states, set to one specific state at a given time. FSMs can be designed in two different ways: as a Moore or Mealy machine. A Moore machine is a state machine whose outputs only depend on the current state. A Mealy machine is a state machine whose outputs depend on both the current state and the input states. Students are tasked with design a vending machine with the following characteristics:

1. The vending machine has 10 different snacks for sale. Each snack has a two-digit code (10-14, 20-24).
2. Each snack is stored in a separate slot. There can be up to 10 units of the snack stored in 1 slot. A counter for every slot keeps track of the number of units of the snack remaining in that slot.
3. A buyer can purchase only 1 item at a time.
4. The machine only accepts payment by card.

 


Figure 1: Vending Machine Display

2 Module Description

For the design of the FSM, I utilized the design specifications to help me plan out my work, with the knowledge of what my inputs and outputs are required to be.

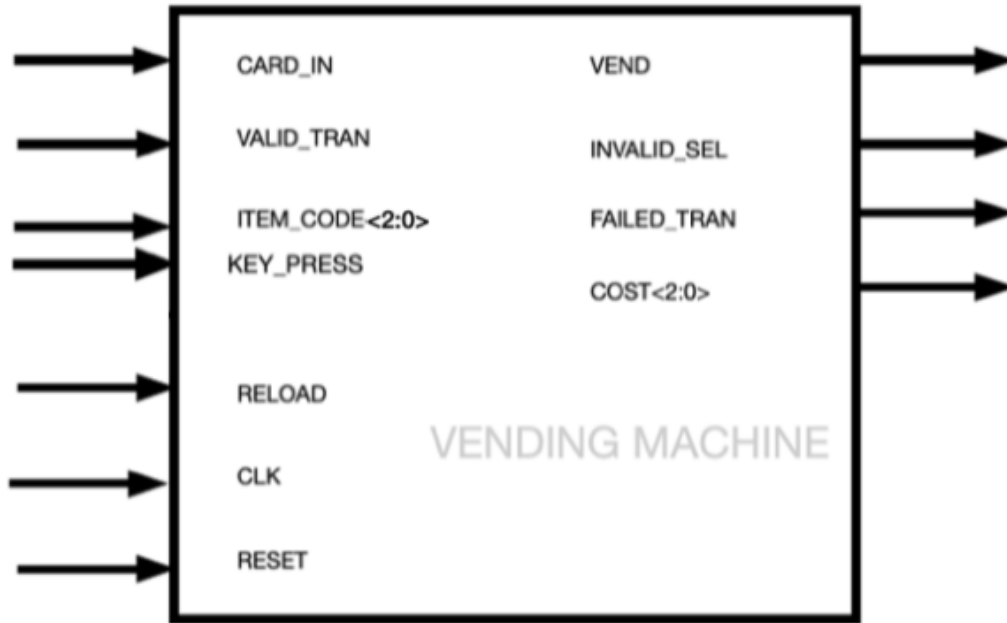


Figure 2: Vending Machine Schematic Overview

Using this "schematic", I created an FSM Moore machine, where my outputs are dependent on the current state.

Descriptions of the states are as explained below:

- When the stRst signal is 1, we set all values 0. When it is 0, we are put in the stIdle state, which waits for inputs such as CARD_IN or stReload. Note that stRst takes precedence over all signals.
- When stReload signal is 1, the count for each slot item is set back to their maximum, which is 10. Afterwards, we are set the state to stIdle.
- While in the stIdle state, if the CARD_IN signal goes to 1, we begin the process of getting inputs for "ordering" in the stCardInsertWait state.

-
- In the `stCardInsertWait` state, we can do two things. First is that, after 5 cycles, if no input is given, we go back to the `stIdle` state. However, if the `KEY_PRESS` signal is 1, we take the `ITEM_CODE` input and store that. In this same state, we wait for another `KEY_PRESS` signal for another `ITEM_CODE` input to complete our 2-digit selection.
 - If the input is invalid, we transition to the `stInvalidIn`, which then goes back to our `stIdle` state.
 - If the input is valid, we go to the `stValidIn` state. In this state, we set the `COST` to the proper value and wait for a `VALID_TRAN` input to be 1. If it is 1, then we transition to the `VEND` state, as the payment has been accepted by the vending machine. If it is 0 for 5 cycles, we go to the `stFailedTran` state.
 - In the `stFailedTran` state, we set the `FAILED_TRAN` output to 1 and go back to the `stIdle` state.
 - In the `stVend` state, the `COST` of the requested item is output and set the `VEND` signal to 1, before setting the state back to `stIdle` after a cycle.


To implement this in Verilog, I created a `vending_machine` module that mimics the schematic from the specifications. Using parameters to create variables to represent all of the necessary states in a specific 4-bit binary encoding, a 4-bit `current_state` and `next_state`, and 4-bit registers to store the count for each item slot in the vending machine.

In Verilog, I utilize always blocks to first update the `current_state`, turn on the 5-cycle timer, or increment the 5-cycle timer. Next, the `next_state` is updated, depending on the current state and inputs. Lastly, I determine what the output should be based on the previous always blocks and output the necessary values.



Figure 3: vending_machine Schematic

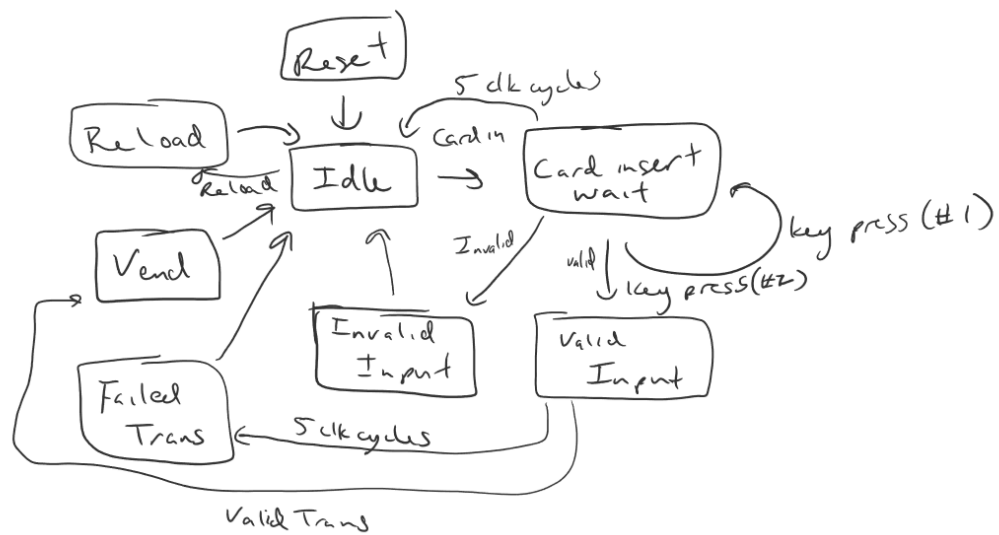Above is the schematic of my vending machine FSM. It looks quite confusing and cluttered, which is the case because of the amount of registers I use, which are updated by counters and manipulated with muxes to get the proper values I desire.



* Reset overrides all arrows,
but not written to avoid extra clutter

Figure 4: vending_machine Schematic Hand-Drawn and Simplified

3 Test-bench Simulation

To test my modules, I tested my main module `vending_machine` and compared the resulting waveforms to the output that I would expect if I had done it in my head. Below are all the test cases waveforms and a short description of what is being tested.

1. Reset Test Waveform: This test simply tested to make sure RESET put all outputs to 0.

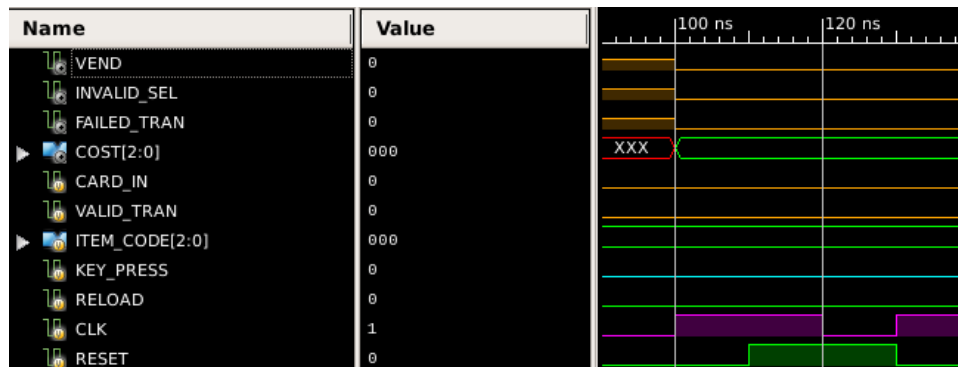


Figure 5: `vending_machine` Reset Test Waveform

2. Reload Test Waveform: This test simply tested to make sure we were able to reload, although this test doesn't affect output, so the waveform is quite trivial.

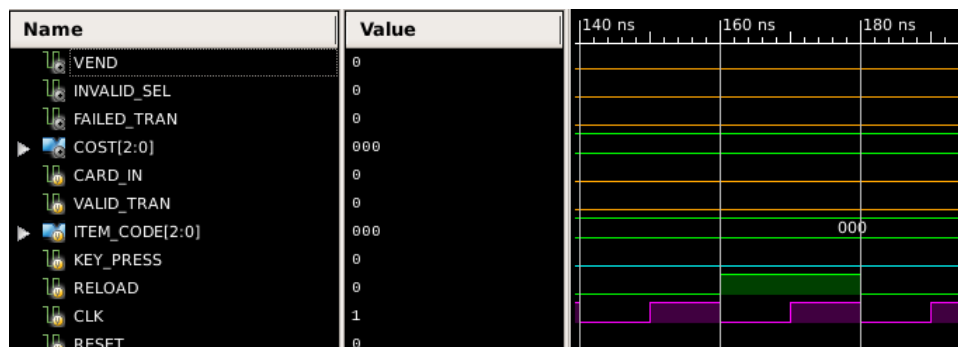


Figure 6: `vending_machine` Reload Test Waveform

3. Normal Test 1 Waveform: This tested to ensure that the normal case worked properly. This one dealt with a item that had a cost of 2, which is properly done, as

shown in the image.

 


Figure 7: vending_machine Normal Test 1 Waveform

4. Normal Test 2 Waveform: This tested to ensure that the normal case worked properly. This one dealt with a item that had a cost of 5, which is properly done, as shown in the image.

 


Figure 8: vending_machine Normal Test 2 Waveform

5. Double Transaction Test Waveform: This tests a transaction stream where CARD_IN stays high through an entire transaction, which would lead to the allowance of another transaction, which is properly done, as shown in the image with 2 high VEND signals.

 


Figure 9: vending_machine Double Transaction Test Waveform

6. Card W/ No Input Test Waveform: This tests that when CARD_IN is high, that

after 5 cycles, it will make INVALID_SEL high for a cycle and then return to idle.

 


Figure 10: vending_machine Card W/ No Input Test Waveform

7. Card W/ 1 Input Test Waveform: This tests that when CARD_IN is high and one ITEM_CODE is inputted, that after 5 cycles, it will make INVALID_SEL high for a cycle and then return to idle.

 


Figure 11: vending_machine Card W/ 1 Input Test Waveform

8. Invalid Code Test Waveform: This test checks to see that when an invalid code (i.e a code that isn't assigned to an item slot), we will get an INVALID_SEL high signal and then return to idle.

 


Figure 12: vending_machine Invalid Code Test Waveform

9. Failed Transaction Test Waveform: This test checks to see that when the vending machine is has all the valid inputs and is waiting more than 5 cycles for a

VALID_TRAN signal to go high, it will make the FAILED_TRAN signal go high and go back to idle.

 


Figure 13: vending_machine Failed Transaction Test Waveform

10. Empty Machine Test Waveform: This test checks to see that when the vending machine is empty and we try to order something, that we will get an INVALID_SEL high signal because there are no more of that item to order.

 


Figure 14: vending_machine Empty Machine Test Waveform

4 Reports

4.1 ISE Design Overview Summary Report

Device Utilization Summary (estimated values)				
Logic Utilization	Used	Available	Utilization	
Number of Slice Registers	58	18224		0%
Number of Slice LUTs	121	9112		1%
Number of fully used LUT-FF pairs	50	129		38%
Number of bonded IOBs	15	232		6%
Number of BUFG/BUFGCTRLs	1	16		6%

Figure 15: Design Summary

Above is the ISE Design Overview Summary Report. As indicated, there are no errors and simply a handful of warnings, which are simply warnings about potential truncation of register values. In addition, it is clear that a ton of registers were utilized, which is as expected.

4.2 Map Report

```
Release 14.7 Map P.20131013 (lin64)
Xilinx Mapping Report File for Design 'vending_machine'

Design Information
-----
Command Line : map -intstyle ise -p xc6slx16-csg324-3 -w -logic_opt off -ol
high -t 1 -xt 0 -register_duplication off -r 4 -global_opt off -mt off -ir off
-pr off -lc off -power off -o vending_machine_map.ncd vending_machine.ngd
vending_machine.pcf
Target Device : xc6slx16
Target Package : csg324
Target Speed : -3
Mapper Version : spartan6 -- $Revision: 1.55 $
Mapped Date : Mon May 24 06:29:34 2021

Design Summary
-----
Number of errors: 0
Number of warnings: 6
Slice Logic Utilization:
  Number of Slice Registers: 60 out of 18,224 1%
    Number used as Flip Flops: 53
    Number used as Latches: 7
    Number used as Latch-thrus: 0
    Number used as AND/OR logics: 0
  Number of Slice LUTs: 105 out of 9,112 1%
    Number used as logic: 104 out of 9,112 1%
      Number using 06 output only: 84
      Number using 05 output only: 0
      Number using 05 and 06: 20
      Number used as ROM: 0
    Number used as Memory: 0 out of 2,176 0%
  Number used exclusively as route-thrus: 1
    Number with same-slice register load: 1
    Number with same-slice carry load: 0
    Number with other load: 0

Slice Logic Distribution:
```

Number of occupied Slices:	42 out of	2,278	1%
Number of MUXCYs used:	0 out of	4,556	0%
Number of LUT Flip Flop pairs used:	111		
Number with an unused Flip Flop:	53 out of	111	47%
Number with an unused LUT:	6 out of	111	5%
Number of fully used LUT-FF pairs:	52 out of	111	46%
Number of unique control sets:	17		
Number of slice register sites lost to control set restrictions:	100 out of	18,224	1%
<p>A LUT Flip Flop pair for this architecture represents one LUT paired with one Flip Flop within a slice. A control set is a unique combination of clock, reset, set, and enable signals for a registered element. The Slice Logic Distribution report is not meaningful if the design is over-mapped for a non-slice resource or if Placement fails.</p>			
IO Utilization:			
Number of bonded IOBs:	15 out of	232	6%
IOB Latches:	6		
Specific Feature Utilization:			
Number of RAMB16BWERs:	0 out of	32	0%
Number of RAMB8BWERs:	0 out of	64	0%
Number of BUFIO2/BUFIO2_2CLKs:	0 out of	32	0%
Number of BUFIO2FB/BUFIO2FB_2CLKs:	0 out of	32	0%
Number of BUFG/BUFGMUXs:	1 out of	16	6%
Number used as BUFGs:	1		
Number used as BUFGMUX:	0		
Number of DCM/DCM_CLKGENs:	0 out of	4	0%
Number of ILOGIC2/ISERDES2s:	0 out of	248	0%
Number of IODELAY2/IODRP2/IODRP2_MCBs:	0 out of	248	0%
Number of OLOGIC2/OSERDES2s:	6 out of	248	2%
Number used as OLOGIC2s:	6		
Number used as OSERDES2s:	0		
Number of BSCANs:	0 out of	4	0%
Number of BUFHs:	0 out of	128	0%
Number of BUFPLLs:	0 out of	8	0%
Number of BUFPLL_MCBs:	0 out of	4	0%

Number of DSP48A1s:	0 out of	32	0%
Number of ICAPs:	0 out of	1	0%
Number of MCBs:	0 out of	2	0%
Number of PCILOGICSEs:	0 out of	2	0%
Number of PLL_ADVs:	0 out of	2	0%
Number of PMVs:	0 out of	1	0%
Number of STARTUPs:	0 out of	1	0%
Number of SUSPEND_SYNCs:	0 out of	1	0%

Average Fanout of Non-Clock Nets: 4.01

Peak Memory Usage: 669 MB
Total REAL time to MAP completion: 26 secs
Total CPU time to MAP completion: 24 secs

Table of Contents

Section 1 - Errors
Section 2 - Warnings
Section 3 - Informational
Section 4 - Removed Logic Summary
Section 5 - Removed Logic
Section 6 - IOB Properties
Section 7 - RPMs
Section 8 - Guide Report
Section 9 - Area Group and Partition Summary
Section 10 - Timing Report
Section 11 - Configuration String Information
Section 12 - Control Set Information
Section 13 - Utilization by Hierarchy

Section 1 - Errors

Section 2 - Warnings

WARNING:Security:42 - Your software subscription period has lapsed. Your current version of Xilinx tools will continue to function, but you no longer qualify for

Xilinx software updates or new releases.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_10_o_Mux_223_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_11_o_Mux_225_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_9_o_Mux_221_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_2_o_Mux_199_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_6_o_Mux_207_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

WARNING:PhysDesignRules:372 - Gated clock. Clock net current_state[3]_GND_5_o_Mux_205_o is sourced by a combinatorial pin. This is not good design practice. Use the CE pin to control the loading of data into the flip-flop.

Section 3 - Informational

INFO:Security:54 - 'xc6slx16' is a WebPack part.

INFO:MapLib:562 - No environment variables are currently set.

INFO:LIT:244 - All of the single ended outputs in this design are using slew rate limited output drivers. The delay on speed critical single ended outputs can be dramatically reduced by designating them as fast outputs.

INFO:Pack:1716 - Initializing temperature to 85.000 Celsius. (default - Range: 0.000 to 85.000 Celsius)

INFO:Pack:1720 - Initializing voltage to 1.140 Volts. (default - Range: 1.140 to 1.260 Volts)

INFO:Map:215 - The Interim Design Summary has been generated in the MAP Report

(.mrp).

INFO:Pack:1650 - Map created a placed design.

Section 4 - Removed Logic Summary

Section 5 - Removed Logic

To enable printing of redundant blocks removed and signals merged, set the detailed map report option and rerun map.

Section 6 - IOB Properties

IOB Name	Type	Direction	IO Standard
CARD_IN	IOB	INPUT	LVCMS25
CLK	IOB	INPUT	LVCMS25
COST<0>	IOB	OUTPUT	LVCMS25
COST<1>	IOB	OUTPUT	LVCMS25
COST<2>	IOB	OUTPUT	LVCMS25
FAILED_TRAN	IOB	OUTPUT	LVCMS25
INVALID_SEL	IOB	OUTPUT	LVCMS25
ITEM_CODE<0>	IOB	INPUT	LVCMS25
ITEM_CODE<1>	IOB	INPUT	LVCMS25
ITEM_CODE<2>	IOB	INPUT	LVCMS25
KEY_PRESS	IOB	INPUT	LVCMS25
RELOAD	IOB	INPUT	LVCMS25
RESET	IOB	INPUT	LVCMS25
VALID_TRAN	IOB	INPUT	LVCMS25
VEND	IOB	OUTPUT	LVCMS25

Section 7 - RPMs

```

-----
Section 8 - Guide Report
-----
Guide not run on this design.

Section 9 - Area Group and Partition Summary
-----

Partition Implementation Status
-----

    No Partitions were found in this design.

-----

Area Group Information
-----

    No area groups were found in this design.

-----

Section 10 - Timing Report
-----
A logic-level (pre-route) timing report can be generated by using Xilinx static
timing analysis tools, Timing Analyzer (GUI) or TRCE (command line), with the
mapped NCD and PCF files. Please note that this timing report will be generated
using estimated delay information. For accurate numbers, please generate a
timing report with the post Place and Route NCD file.

For more information about the Timing Analyzer, consult the Xilinx Timing
Analyzer Reference Manual; for more information about TRCE, consult the Xilinx
Command Line Tools User Guide "TRACE" chapter.

Section 11 - Configuration String Details
-----
Use the "-detail" map option to print out Configuration Strings


Section 12 - Control Set Information
-----
Use the "-detail" map option to print out Control Set Information.

Section 13 - Utilization by Hierarchy
-----
Use the "-detail" map option to print out the Utilization by Hierarchy section.

```

Above is my Map Report. Although there is a lot of details, I can see that just like in the Synthesis Report, we are using a large amount of registers, although not anywhere near the maximum number of registers possible that I could use. In addition, there a handful of warnings which notify me of my bad practices that I wasn't even aware of myself, nor do I know much about how to fix them. Luckily however, it doesn't affect my code and the outputs of it, and simply is a practice I should not use in the future.

5 Conclusion

In this lab, I designed a FSM vending machine, based on a Moore machine. I implemented a wide variety of topics discussed in lecture, including the use of parameters and a switch-case statement.

There were quite a few difficulties that I ran into. The more prominent ones included trying to get the 5 clock cycles to line up properly. How I implemented my code, I actually had to take into consideration the time to process the changes in signals after, say, a KEY_PRESS signal went low. In addition, I wasn't sure how to implement the steady clock in this code. I feel that I could have, but instead, I just had a bunch of `#10` delays, which made timing too difficult.